



به نام خدا



دانشگاه تهران

پردیس دانشکده‌های فنی

دانشکده مهندسی برق و کامپیوتر

سیستم‌های دیجیتال 1

استاد: دکتر نوابی


تمرین کامپیوتری شماره 6

فرید سیاه‌کلی


شماره دانشجویی: 810198510

فروردین 1400

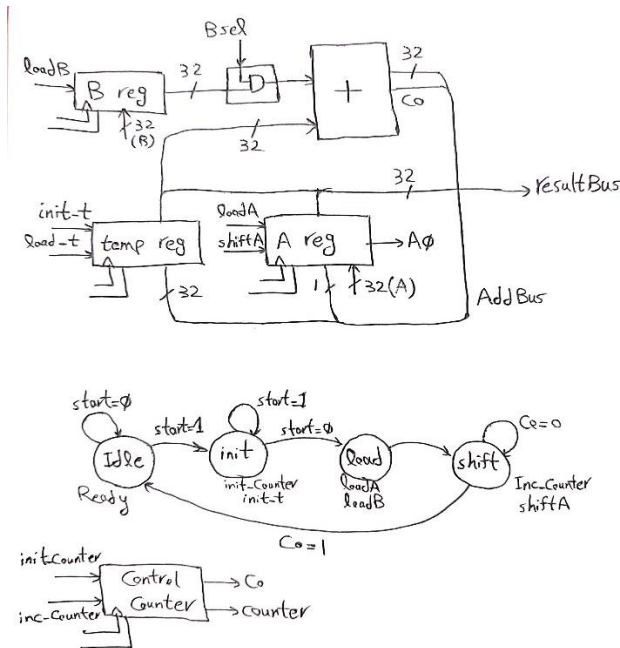
شکل Sequential Multiplier برای Controller و Datapath




شکل Input Wrapper برای Controller

 


شکل Input Wrapper برای Datapath

 

شکل Output Wrapper برای Datapath

 

شکل Controller برای Output Wrapper:

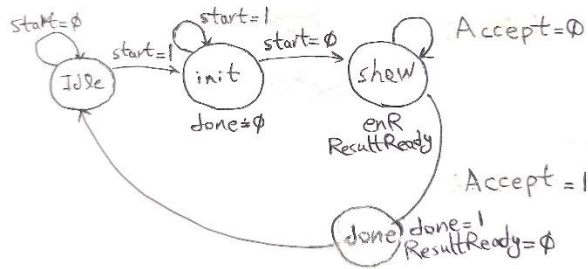

کد وریلاگ Sequential Multiplier:

```

timescale 1ns/1ns
module MULTDP(input clk, rst, loadA, loadB, loadP, shiftA, InitP, Bsel,
  input [23:0] Abus, BBus, output [47:0] ResultBus, output A0);
  reg [23:0] Areg, Breg, Preg;
  wire [23:0] B_AND;
  wire [25:0] AddBus;
  always @(posedge clk, posedge rst) begin
    if (rst) Breg <= 24'b0;
    else if (loadB) Breg <= BBus;
  end
  always @(posedge clk, posedge rst) begin
    if (rst) Preg <= 24'b0;
    else begin
      if (InitP) Preg <= 24'b0;
      else if (loadP) Preg <= AddBus [25:1];
    end
  end
  always @(posedge clk, posedge rst) begin
    if (rst) Areg <= 24'b0;
    else begin
      if (loadA) Areg <= Abus;
      else if (shiftA) Areg <= {AddBus[0], Areg[23:1]};
    end
  end
  assign B_AND = Bsel ? Breg : 24'b0;
  assign AddBus = B_AND + Preg;
  assign ResultBus = {Preg, Areg};
  assign A0 = Areg[0];
endmodule

module MULTCU(input clk, rst, start, A0, output reg loadA, shiftA, loadB, loadP, InitP, Bsel, ready);
  wire Co;
  reg Init_counter, Inc_counter;
  reg [1:0] pstate, nstate;
  reg [4:0] Count;
  parameter [1:0] Idle = 0, Init = 1, load = 2, shift = 3;
  always @(pstate, start, A0, Co) begin
    nstate=0;
    {loadA, shiftA, loadB, loadP, InitP, Bsel, ready} = 7'b0;
    {Init_counter, Inc_counter} = 2'b0;
    case(pstate)
      Idle: begin nstate = start ? Init : Idle; ready = 1'b1; end
      Init: begin nstate = start ? Init : load; Init_counter = 1'b1; InitP = 1'b1; end
      load: begin nstate = shift; loadA = 1'b1; loadB = 1'b1; end
      shift: begin nstate = Co ? Idle : shift; loadP = 1'b1; shiftA = 1'b1; Inc_counter = 1'b1; Bsel = A0; end
      default: nstate = Idle;
    endcase
  end
  always @(posedge clk, posedge rst) begin
    if (rst) pstate <= Idle;
    else pstate <= nstate;
  end
  always @(posedge clk, posedge rst) begin
    if (rst) Count <= 3'b0;
    else if (Init_counter) Count <= 4'b1000;
    else if (Inc_counter) Count <= Count + 1;
  end
  assign Co = &Count;
endmodule

```

کد وریلاگ Input Wrapper:

```

module Input_wrapper(input clk, rst, inReady, inAccept, output reg enA, enB);
    integer counter = 0;
    always @(posedge clk, posedge rst) begin
        if(rst) begin
            enA <= 1'b1;
            enB <= 1'b0;
            counter = 0;
        end
        else if(inReady & ~inAccept & ~counter) begin
            enA <= ~enA;
            enB <= ~enB;
            counter = 1;
        end
    end
end

endmodule

module register32(input [31:0] Parallel_in, input clk, rst, enable, output reg [31:0] parallel_out, input Ready, output reg Accepted);
    always @(posedge clk, posedge rst) begin
        if(rst) begin
            parallel_out <= 32'd0;
            Accepted <= 0;
        end
        else if(Ready & enable) begin
            parallel_out <= Parallel_in;
            Accepted = 1;
        end
        else Accepted <= 0;
    end
end
endmodule

```

کد وریلاگ Output Wrapper:

```

module Output_Wrapper(input clk, rst, input [9:0] Resultexpfinal, input [22:0] product_mantissa, input Sign, doneMul,
    output reg [31:0] ResultBus, input resultaccepted, output reg resultready, Operationdone, enR);
    always @(posedge clk, posedge rst) begin
        if(rst) begin
            resultready <= 0;
            Operationdone <= 0;
        end
        else if(resultaccepted) begin
            resultready <= 0;
            Operationdone = 1;
        end
        else if(doneMul & ~Operationdone) begin
            enR = 1;
            resultready <= 1;
            ResultBus <= {Sign, Resultexpfinal[7:0], product_mantissa};
        end
        else resultready <= 0;
    end
end
endmodule

```

کد وریلاگ Top Level:

```


module Multiplier_32bit_TOP_PRE(input clk, rst, startMul, input [31:0] IN, output [31:0] ResultBusOut,
    input inReady, output Accept, input resultaccepted, output resultready);
    wire A0, loadA, shiftA, loadB, loadP, InitP, Bsel;
    wire enA, enB, Accept1, Accept2, Co, Col, Sign, Operationdone, enR;
    wire [47:0] ResultMul, product_normalised;
    wire [22:0] product_mantissa;
    wire [31:0] A, B, ResultBus;
    wire [9:0] Resultexp, Resultadder, Resultexpfinal;
    Input_wrapper IW(clk, rst, inReady, Accept, enA, enB);
    register32 Areg(IN, clk, rst, enA, A, inReady, Accept1);
    register32 Breg(IN, clk, rst, enB, B, inReady, Accept2);
    assign Accept = Accept1 | Accept2;
    MULTDP dp(clk, rst, loadA, loadB, loadP, shiftA, InitP, Bsel, {1'b1,A[22:0]}, {1'b1,B[22:0]}, ResultMul, A0);
    MULTCU cu(clk, rst, startMul, A0, loadA, shiftA, loadB, loadP, InitP, Bsel, doneMul);
    adder8bit add(A[30:23], B[30:23], 1'b0, Resultadder, Co);
    adder10bit subtract(Resultadder, {10'b1000000010}, 1'b0, Resultexp, Col);
    SignDetector signdetect(A[31], B[31], Sign);
    Normalizer Norm(ResultMul, Resultexp, product_mantissa, Resultexpfinal);
    Output_Wrapper OW(clk, rst, Resultexpfinal, product_mantissa, Sign, doneMul, ResultBus, resultaccepted, resultready, Operationdone, enR);
    register32out Rreg(ResultBus, clk, rst, enR, ResultBusOut);
endmodule

```

تست بنچ مربوطه:

```
`timescale 1ns/1ns
module Multiplier_32bit_TB();
    reg clk='b0, rst = 0, start = 0, inReady = 0, resultAccepted = 0, inReady2 = 0, resultAccepted2 = 0;
    wire inAccept, resultReady, inAccept2, resultReady2;
    reg [31:0] inBus, outBus_pre, outBus_post;
    wire [31:0] out1, out2;
    Multiplier_32bit_TOP_PRE UUT1(clk, rst, start, inBus, out1, inReady, inAccept, resultAccepted, resultReady);
    Multiplier_32bit_TOP UUT2(clk, rst, start, inBus, out2, inReady2, inAccept2, resultAccepted2, resultReady2);
    always #5 clk <= ~clk;
    initial begin
        #20 rst=1;
        #20 rst=0;
        #20 inBus = 32'b10111110100110011001100110011010;
        #20 inReady = 1; inReady2 = 1;
        #20 if(inAccept) begin inReady = 0; end
        if(inAccept2) begin inReady2 = 0; end
        #20 inBus = 32'b01000011111101000100000000000000;
        #20 inReady = 1; inReady2 = 1;
        #20 if(inAccept) inReady = 0;
        if(inAccept2) inReady2 = 0;
        #20 start=1;
        #20 start=0;
        #300;
        #20 if(resultReady) begin
            outBus_pre = out1;
            resultAccepted = 1;
        end
        if(resultReady2) begin
            outBus_post = out2;
            resultAccepted2 = 1;
        end
        #30 if(~resultReady) resultAccepted = 0;
        if(~resultReady2) resultAccepted2 = 0;
        #30
        #0 $stop;
    end
endmodule
```

 برای تست کردن ماژول ضرب Sequential، تست بنچی درست کردیم که درستی خروجی تایید شود:




حال با استفاده از کوارتز، کد سنتز شده و خروجی‌های .vo و .sdo که شامل دیلی‌های ماژول است دریافت

شده و در پایان کد اولیه و کد سنتز شده در کنار هم اجرا شده‌اند تا تفاوت قابل مشاهده باشد.


(از آنجا که در این شبیه‌سازی، مقادیر ورودی و خروجی رپ‌های input و output همگی مشخص هستند،

دیگر تست بنچی جدا برایشان نوشته نشد و همینجا کارکرد آنها را می‌توان بررسی کرد)


شکل موج خروجی:

 


رسم RTL view ماژول:

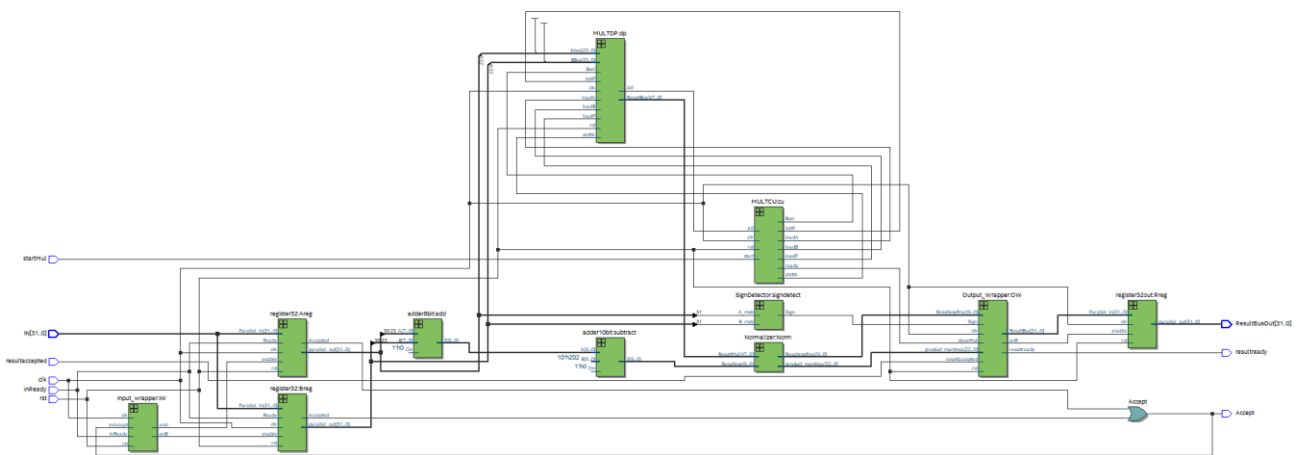

بلاک دیاگرام Sequential Multiplier:

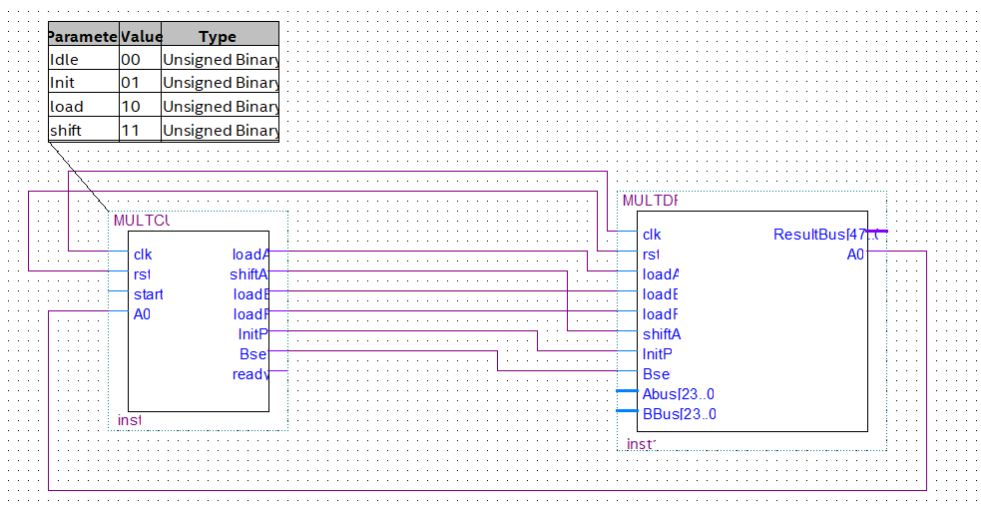

بلاک دیاگرام Top Level :

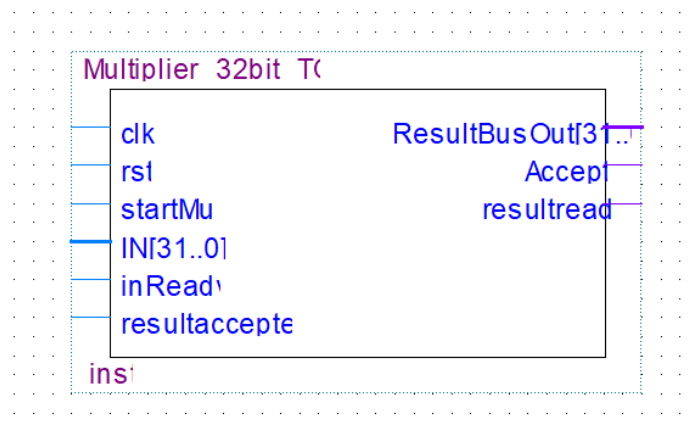

بلاک دیاگرام Wrappers :

